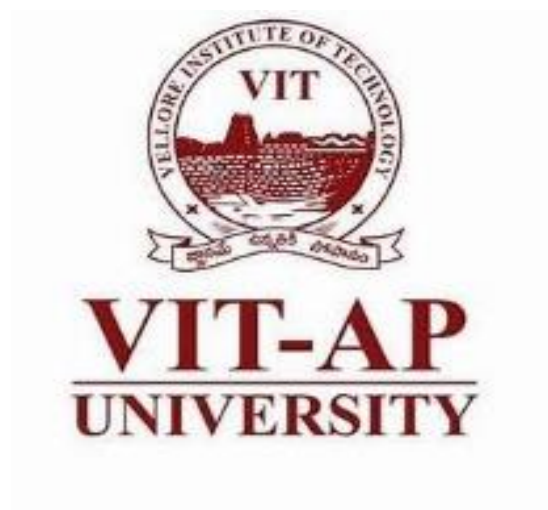


# **LAB REPORT**

## **Fundamentals of Electrical and Electronics Engineering Lab**

**By**

**MAJJIGA JASWANTH  
20BCD7171**



## **INDEX**

### **EXPERIMENTS**

- 1. ANALYSIS OF RESISTANCE USING COLOUR CODING**
- 2. VERIFICATION OF OHM'S LAW**
- 3. VERIFICATION OF KCL AND KVL**
- 4. VERIFICATION OF CURRENT AND VOLTAGE DIVISION RULE**
- 5. VERIFICATION OF VOLTAGE CURRENT POWER RELATIONS FOR STAR DELTA CONNECTED LOADS**
- 6. CALCULATION OF TWO PORT NETWORK PARAMETERS**
- 7. STUDY OF CHARACTERISTICS OF SEMICONDUCTOR DIODE TRANSISTORS**
- 8. DESIGN AND SIMULATION OF VARIOUS RECTIFIER CIRCUITS**
- 9. DESIGN AND IMPLEMENTATION OF MOSFET VOLTAGE AMPLIFIER**
- 10. APPLICATION OF THEVENIN'S THEOREM**

## **Experiment 1**

### **ANALYSIS OF RESISTANCE USING COLOR CODING**

#### **Objectives :**

1. To learn Resistor color code
2. To determine the stated value of a resistor by interpreting the colour code indicated on the resistor.

**Software Used : Ni Multisim 14.0**

**Theory :** The resistors used in laboratory are carbon composition resistors, consisting of graphite or some other type of carbon embedded in a filler material. Graphite is a moderately good conductor, so by varying the graphite-filler mix, a large range of resistance values can be obtained (the less graphite, the higher the resistance). Carbon resistors are cheap and reliable, however, their tolerances (5 to 20% deviation from nominal values) indicate that larger errors can be expected. Other types of resistors include wire wound, metal film, and carbon film. The nominal value and tolerance of a carbon resistor can be determined from the color-coded stripes that appear on the resistor. The first three bands represent the two significant figures of the resistance, while the fourth band indicated the number of zeros that follow. If there are only three bands, the resistor has a 20% tolerance. If the three color bands are followed by a silver band, the resistor has a 10% tolerance. A gold band following the three color bands indicates a 5% tolerance, a red band indicates a 2% tolerance, and a brown band indicates a 1% tolerance.

## Circuit Diagram :

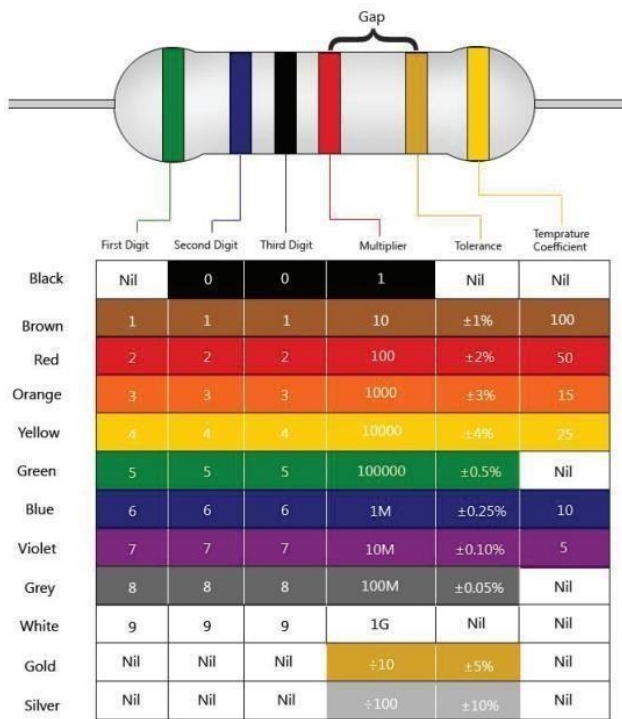


Figure 1: Colour code for a resistor.

## Result & Observation :

	Resistance Value	Tolerance
	$22 \times 10^2 \Omega$	±5%
	$56 \times 10^4 \Omega$	±10%
	$47 \times 10^3 \Omega$	±10%
	$10 \times 10^1 \Omega$	±5%

## EXPERIMENT 2


### VERIFICATION OF OHM'S LAW

**Objective:** To verify Ohm's Law

**Software Used:** NI Multisim 14.0

**Theory:** Ohm's law states that the voltage or potential difference between two points is directly proportional to the current or electricity passing through the resistance, and directly proportional to the resistance of the circuit. The formula for Ohm's law is  $V=IR$ . This relationship between current, voltage, and relationship was discovered by German scientist Georg Simon Ohm. Let us learn more about Ohms Law, Resistance, and its applications.

**Circuit Diagram:**

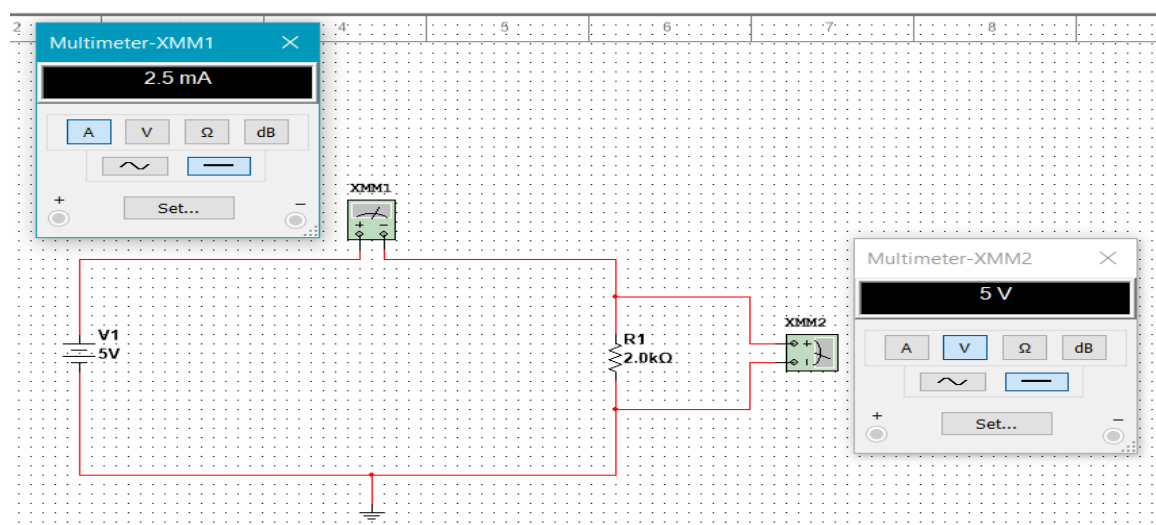

**Result & Observations :**

S. No	Source Voltage (V)	Resistance $k\Omega$	Theoretical		Experimental	
			Current (A)	Voltage Out(V)	Current	Voltage Out(V)
1	5	1	$5 \times 10^{-3}$	5	5mA	5
2	5	2	$2.5 \times 10^{-3}$	5	2.5mA	5
3	5	3	$0.1 \times 10^{-3}$	3	1mA	3
4	5	4	$0.5 \times 10^{-3}$	2	500 $\mu$ A	2
5	5	5	$0.4 \times 10^{-3}$	2	400 $\mu$ A	2

Hence we can see the values of theoretical and experimental are matched we can say ohms law is verified.

## EXPERIMENT 3

**Objective:** To verify Kirchhoff's current law(kcl) in the circuit

**Software used:** NI MULTISIM 14.0.

### THEORY:

1. Kirchhoff's Current Law or KCL, states that the "total current or charge entering a junction or node is exactly equal to the charge leaving the node as it has no other place to go except to leave, as no charge is lost within the node ". In other words, the algebraic sum of ALL the currents entering and leaving a node must be equal to zero,  $I(\text{exiting}) + I(\text{entering}) = 0$ . This idea by Kirchhoff is commonly known as the Conservation of Charge.


2. Here, the three currents entering the node,  $I_1, I_2, I_3$  are all positive in value and the two currents leaving the node,  $I_4$  and  $I_5$  are negative in value. Then this means we can also rewrite the equation as;

3.  $I_1 + I_2 + I_3 - I_4 - I_5 = 0$

4. The term Node in an electrical circuit generally refers to a connection or junction of two or more current carrying paths or elements such as cables and components. Also, for current to flow either in or out of a node a closed-circuit path must exist. We can use Kirchhoff's current law when analyzing parallel circuits

**Circuit 1:** Connect three resistors in parallel and one resistor in series and connect the multimeter for each of the resistor to note down values of individual resistor

### Circuit diagram:

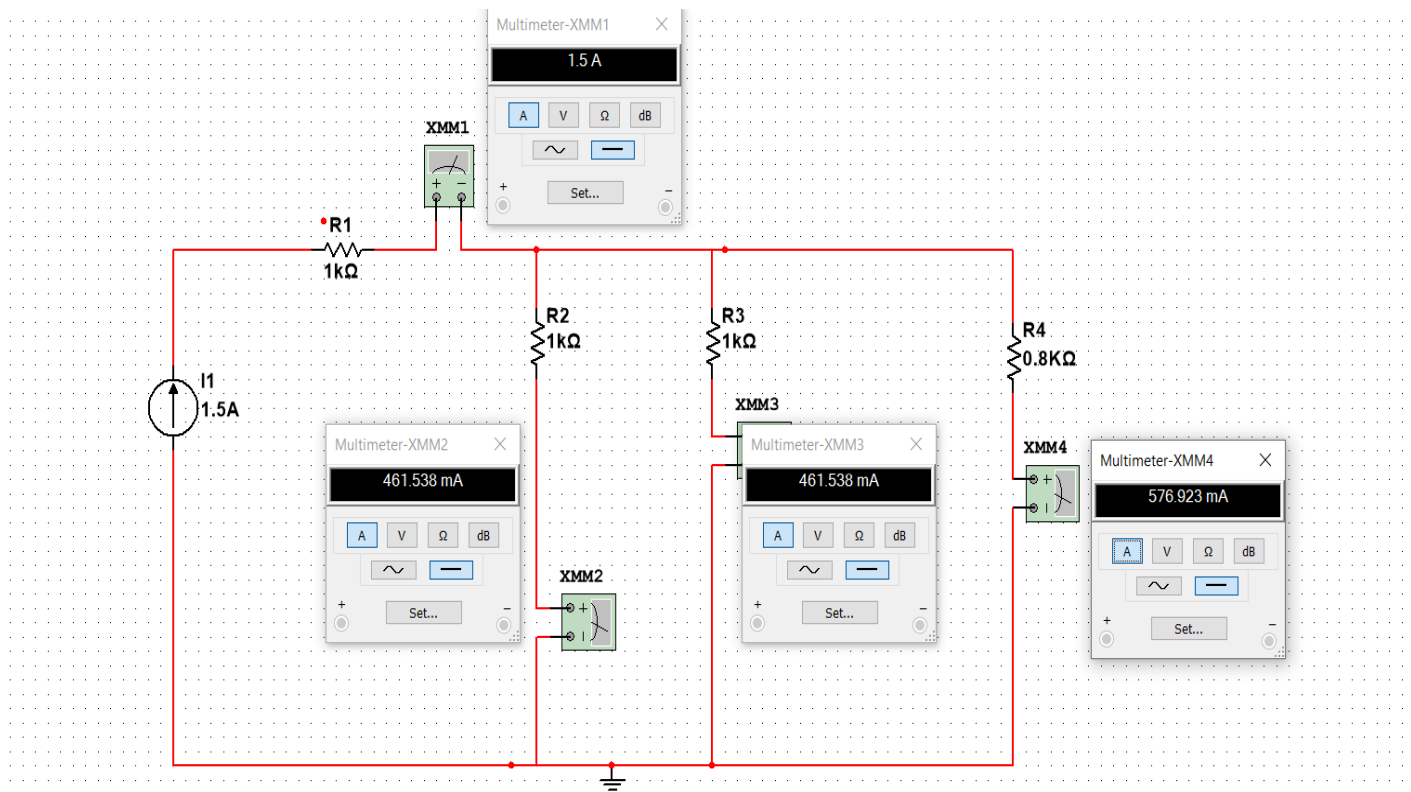

### Observation:

Current through the resistors  $R_1$ ,  $R_2$ ,  $R_3$ ,  $R_4$  are 1.5A, 461.538 mA, 461.538 mA, 576.923 mA respectively.

### Significance:

The law states that at any circuit junction, the sum of the currents flowing into and out of that junction are equal. In simple terms, what KCL really says is that, the sum of all currents entering a node is equal to the sum of all currents leaving the node.



**Result:**

1. The sum of currents entering and leaving are equal at the node
2. In circuit  $I = I_1 + I_2 + I_3$
3. Hence the values are known for the equation  $I = I_1 + I_2 + I_3$   
 $1.5A = 461.538mA + 461.538mA + 576.923mA$
4. Now the Kirchhoff current law has been verified

**Objective:** To verify Kirchhoff's voltage law (kvl) in the circuit

**Software used:** NI MULTISIM 14.0 **Theory:**


1. Gustav Kirchhoff's Voltage Law is the second of his fundamental laws we can use for circuit analysis. His voltage law states that for a closed loop series path the algebraic sum of all the voltages around any closed loop in a circuit is equal to zero. This is because a circuit loop is a closed conducting path so no energy is lost
2. In other words, the algebraic sum of ALL the potential differences around the loop must be equal to zero as:  $\sum V = 0$ . Note here that the term "algebraic sum" means to take into account the polarities and signs of the sources and voltage drops around the loop.
3. This idea by Kirchhoff is commonly known as the Conservation of Energy, as moving around a closed loop, or circuit, you will end up back to where you started in the circuit and therefore back to the same initial potential with no loss of voltage around the loop. Hence any voltage drops around the loop must be equal to any voltage sources met along the way

### Circuit 2:

Connect three resistors in series and connect the multimeter parallel to each of the resistor to note the individual voltage value

- Connect three resistors in parallel and multimeters to it in parallel
- And connect a voltage  $V1 = 10\text{v}$  and give the resistor values as follow
- $R1 = 5\text{v}$ ,  $R2 = 3\text{v}$ ,  $R3 = 2\text{v}$

**Circuit diagram:**

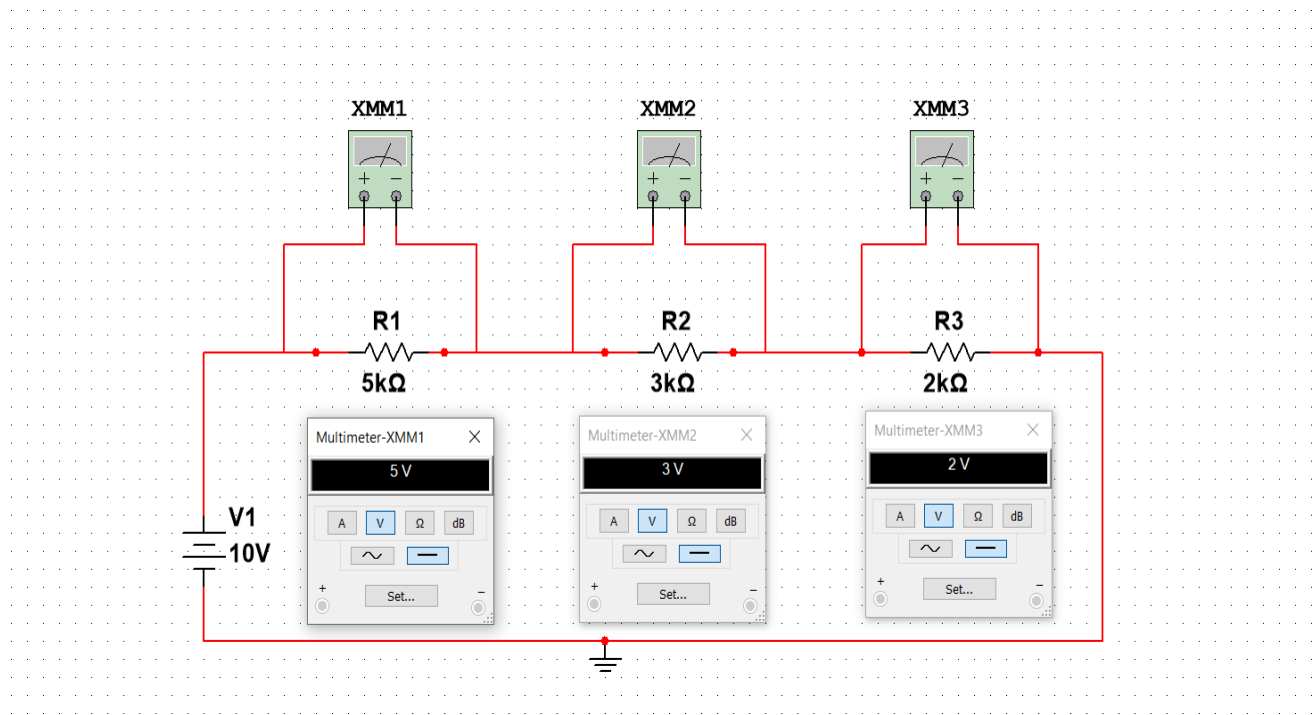

### Observation:

Voltage across the resistors  $R1$ ,  $R2$ ,  $R3$  are 5v, 3v, 2v respectively

Voltage given is 10v so that sum of voltages of their respective voltages should be equal

$$V = V_1 + V_2 + V_3$$

$$5v + 3v + 2v = 10v$$

**Significance:**

Kirchhoff's loop rule (otherwise known as Kirchhoff's voltage law (KVL), Kirchhoff's mesh rule, Kirchhoff's second law, or Kirchhoff's second rule) is a rule pertaining to circuits, and is based on the principle of conservation of energy.

**Result:**

The algebraic sum of all voltages around any closed loop in a circuit is zero

Now Kirchhoff's voltage law has been verified

## EXPERIMENT 4

### VERIFICATION OF CURRENT AND VOLTAGE DIVISION RULE

**Objective:** To verify current and voltage division rule

**Software Used:** NI Multisim 14.0

#### Theory:


**Voltage Division Rule:** The **voltage** across any resistor in a series connection of resistors shall be equal to the ratio of the value of the resistor divided by the equivalent resistance of the circuit. This is called **Voltage division rule**.  $V_{out} = (V_s * R_2) / (R_1 + R_2)$



**Current Division Rule:** Parallel circuits in which the source or supply current divides into a number of parallel paths. In a parallel connected circuit, all the components have their terminals connected together sharing the same two end nodes. This results in different paths and branches for the current to flow or pass along. However, the currents can have different values through each component.

The main characteristic of parallel circuits is that while they may produce different currents flowing through different branches, the voltage is common to all the connected paths. That is  $V_{R1} = V_{R2} = V_{R3} \dots$  etc. Therefore, the need to find the individual resistor voltages is eliminated allowing branch currents to be easily found with Kirchhoff's Current Law, (KCL) and of course Ohm's Law.

$$I_2 = I_s * R_2 / R_1 + R_2$$

**Circuit Diagram:**

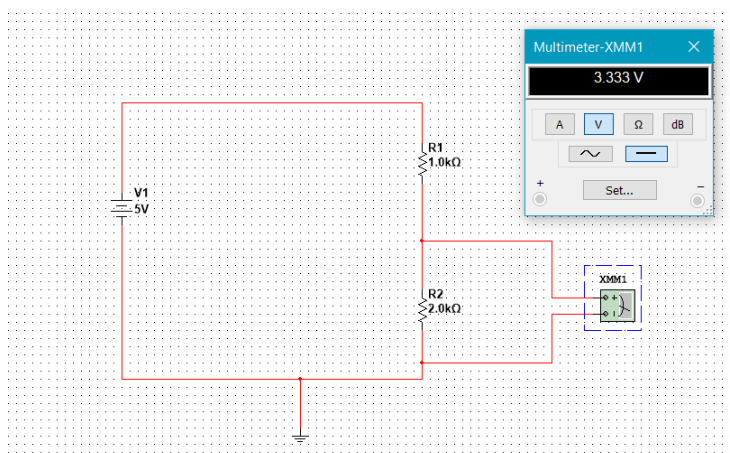

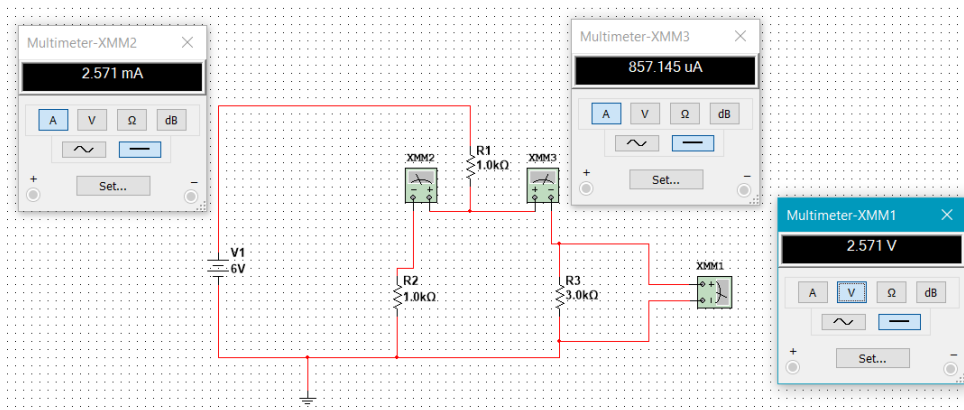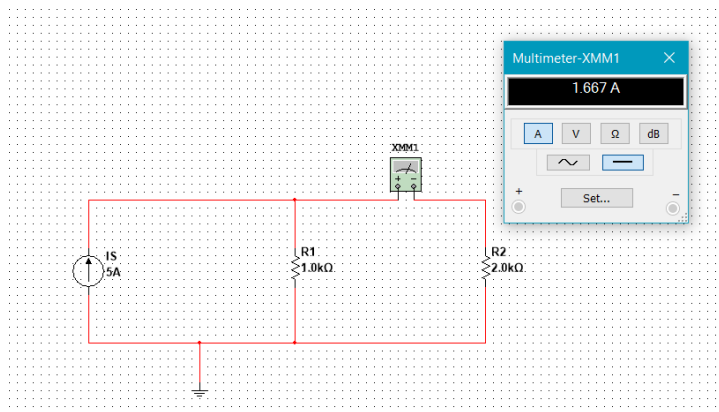

### Result & Observations:

- Voltage Division Rule:**

S No.	Source Voltage (V)	Resistance 1 kΩ	Resistance 2 kΩ	Theoretical Voltage Out (V)	Experimental Voltage Out (V)
1	5	1	2	3.33	3.33
2	5	2	3	3	3
3	5	2.5	3.1	2.76	2.76
4	5	2.6	3.2	2.75	2.75
5	5	3	5.25	3.18	3.18

- Current Division Rule:**

S No.	Source Voltage (V)	Resistance 1 kΩ	Resistance 2 kΩ	Theoretical Voltage Out (V)	Experimental Voltage Out (V)
1	5	1	2	1.66	1.66
2	5	2	3	2	2
3	5	2.5	3.1	2.23	2.23
4	5	2.6	3.2	2.24	2.24
5	5	3	5.25	1.81	1.81

				Theoretical	Experimental
S No.	Source Voltage (V)	Current I1 (A)	Current I2 (A)	Voltage Out (V)	Voltage Out (V)
1	5	$2.1 \times 10^{-3}$	$0.714 \times 10^{-3}$	2.142	2.143
2	6	$2.55 \times 10^{-3}$	$0.857 \times 10^{-3}$	2.571	2.571
3	7	$3 \times 10^{-3}$	$1 \times 10^{-3}$	3	3

Hence theoretical and experimental values are matched we can say voltage and current division rule is verified

## **EXPERIMENT-5**

### **VERIFICATION OF VOLTAGE CURRENT POWER RELATIONS FOR STAR AND DELTA CONNECTED LOADS**

**Objective:** To verify the voltage, current, power relations for star and delta connected loads

**Software Used:** NI MULTISIM 14.0

**Theory:**

**Voltages and currents in Y-connection:**

- The voltage induced in each winding is called the phase voltage and current in each winding is likewise known as phase current.
- However, the voltage available between any pair of terminals is called line voltage (VL) and the current flowing in each line is called line current (IL).

**Line voltage and phase voltage:**

- The conductors between a voltage source and a load are called lines, and the voltage between any two lines is called line voltage.
- The voltage measured between any line and neutral is called phase voltage.
- The p.d. between line 1 and 2 is  $V_{RY} = E_R - E_Y$ .
- Hence,  $V_{RY}$  is found by compounding  $E_R$  and  $E_Y$  reversed.
- Obviously, the angle between  $E_R$  and  $E_Y$  reversed is  $60^\circ$ . Hence if  $E_R = E_Y = E_B =$  say,  
 $E_{ph}$  the phase e.m.f.,
- Then  $V_{RY} = 2 \times E_{ph} \cos (60^\circ/2)$   
 $= \sqrt{3}E_{ph}$  similarly,  $V_{YB} = E_Y - E_B = \sqrt{3}E_{ph}$   
and  $V_{BR} = E_B - E_R = \sqrt{3}E_{ph}$
- Now  $V_{RY} = V_{YB} = V_{BR} =$  line voltage, say VL. Hence, in star connection  $V_L = \sqrt{3}E_{ph}$

**Line currents and phase currents:**

- Line current in each line is the same as the current in the phase winding to which the line is connected.
- Current in line 1 =  $I_R$ ; Current in line 2 =  $I_Y$ ;
- Current in line 3 =  $I_B$  Since  $I_R = I_Y = I_B =$  say,

- $I_{ph}$  = the phase current
- Line current  $I_L = I_{ph}$ .

**Power:**

- The total active or true power in the circuit is the sum of the three phase powers.
- Total active power =  $3 \times \text{phase power}$  or  $P = 3 \times V_{ph} I_{ph} \cos \phi$   $P = \sqrt{3} V_L I_L \cos \phi$

**Delta ( $\Delta$ ) or Mesh Connection:**

- If the system is balanced then sum of the three voltages round the closed mesh is zero.
- This type of connection is also referred to as 3-phase, 3-wire system.

**Line Voltages and Phase Voltages:** The voltage between lines 1 and 2 as  $V_{RY}$  and that between lines 2 and 3 as  $V_{YB}$ , we find that  $V_{RY}$  lead  $V_{YB}$  by  $120^\circ$ . Similarly,  $V_{YB}$  leads  $V_{BR}$  by  $120^\circ$ . Let  $V_{RY} = V_{YB} = V_{BR} = \text{line voltage } V_L$ . Then, it is seen that  $V_L = V_{ph}$

**Line Currents and Phase Currents:** Current in each line is the vector difference of the two phase currents flowing through that line. Current in line No. 1 is found by compounding  $I_R$  and  $I_B$  reversed  $I_1 = 2 \times I_{ph} \times \cos (60^\circ/2) = \sqrt{3} I_{ph}$

$$I_2 = I_B - I_Y =$$

$$\sqrt{3} I_{ph} \quad I_3 =$$

$$I_B - I_Y =$$

$$\sqrt{3} I_{ph}$$

Since all the line currents are equal in magnitude



$$\text{i.e. } I_1 = I_2 = I_3 = I_L$$

$$I_L = \sqrt{3} I_{ph}$$

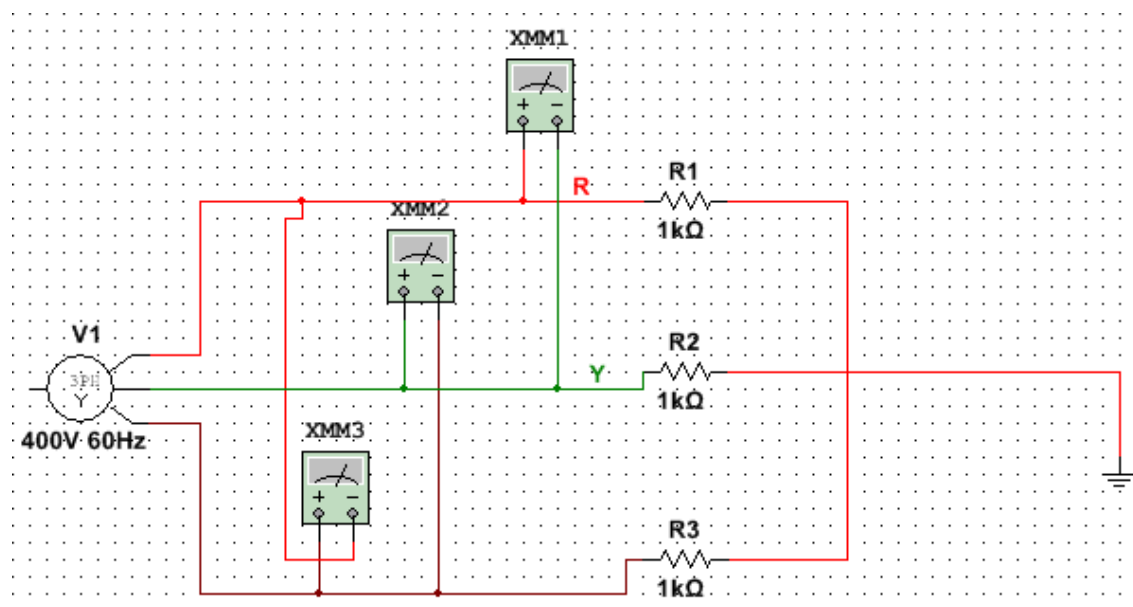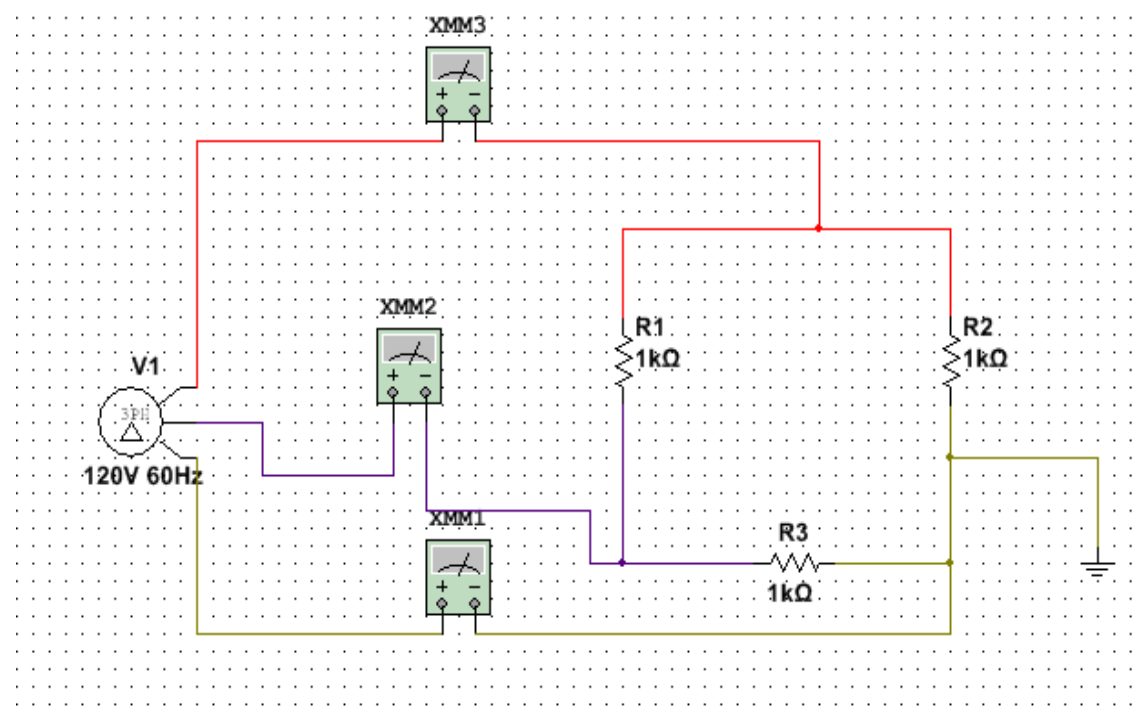**Power:**

$$\text{Total power} = 3 \times V_{ph} I_{ph} \cos \phi$$



**Star connected load:****Delta connected load:**

**Result and observation:****Star connected load:**

	MULTISIM VALUE	THEORITICAL VALUE
V <sub>RY</sub>	692.872V	692.8V
V <sub>YB</sub>	692.872V	692.8V
V <sub>BR</sub>	692.872V	692.8V
I <sub>R</sub>	400.03mA	400 mA
I <sub>Y</sub>	400.016 mA	400mA
I <sub>b</sub>	400.023 mA	400mA
P <sub>1</sub>	240.037W	240 W
P <sub>2</sub>	240.037W	240 W
P = p <sub>1</sub> +p <sub>2</sub>	480.074W	480.07W

**Delta connected load:**

	MULTISIM VALUE	THEORITICAL VALUE
V <sub>RY</sub>	400V	400V
V <sub>YB</sub>	400V	400V
V <sub>BR</sub>	400V	400V
I <sub>R</sub>	692.861mA	692.8mA
I <sub>Y</sub>	692.872mA	692.8mA
I <sub>b</sub>	692.848mA	692.8mA
P <sub>1</sub>	240.037W	
P <sub>2</sub>	240.037W	
P = p <sub>1</sub> +p <sub>2</sub>	480.074W	480W

As we can see both theoretical values are same therefore the values are verified

## Experiment- 6

### CALCULATION OF TWO PORT NETWORK PARAMETERS

#### Objective :

- To understand the analysis of a two-port network.
- To understand the behavior of a two-port network using parametric analysis.
- To learn the conditions and procedure for two-port analysis.measurement

Software Used : NI Multisim 14.0

**Theory :** The electrical network with two pairs of terminals is a two-port network. The network can contain resistors, inductors, capacitors, transformers, transistors and in general any linear circuit device, including depending devices but no independent sources are allowed. The behavior of a linear two-port network is described by impedance (Z), admittance (Y), transmission (ABCD), or hybrid (h) parameter.

#### Z Parameter :

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

Parameter	Condition	Name
$Z_{11}=V_1/I_1$	$I_2=0$	Input impedance
$Z_{21}=V_2/I_1$	$I_2=0$	Transfer impedance
$Z_{12}=V_1/I_2$	$I_1=0$	Transfer impedance
$Z_{22}=V_2/I_2$	$I_1=0$	Output impedance

#### Y Parameter :

$$I_1 = Y_{11} V_1 + Y_{12} V_2$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2$$

Parameter	Condition	Name
$Y_{11}=I_1/V_1$	$V_2=0$	Input admittance
$Y_{21}=I_2/V_1$	$V_2=0$	Transfer admittance
$Y_{12}=I_1/V_2$	$V_1=0$	Transfer admittance
$Y_{22}=I_2/V_2$	$V_1=0$	Output admittance

**H Parameter :**

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$


Parameter	Condition	Name
$h_{11}=V_1/I_1$	$V_2=0$	SS input admittance
$h_{21}=I_2/I_1$	$V_2=0$	SS forward current gain
$h_{12}=V_1/V_2$	$I_1=0$	OS reverse voltage gain
$h_{22}=I_2/V_2$	$I_1=0$	OS output admittance

**ABCD Parameter :**

$$V_1 = A V_2 - B I_2$$

$$I_1 = C V_2 - D I_2$$

Parameter	Condition	Name
$A=V_1/V_2$	$I_2=0$	OC voltage ratio
$B=V_1/-I_2$	$V_2=0$	OC transfer admittance
$C=I_1/V_2$	$I_2=0$	-SC transfer impedance
$D=I_1/-I_2$	$V_2=0$	-SC current ratio

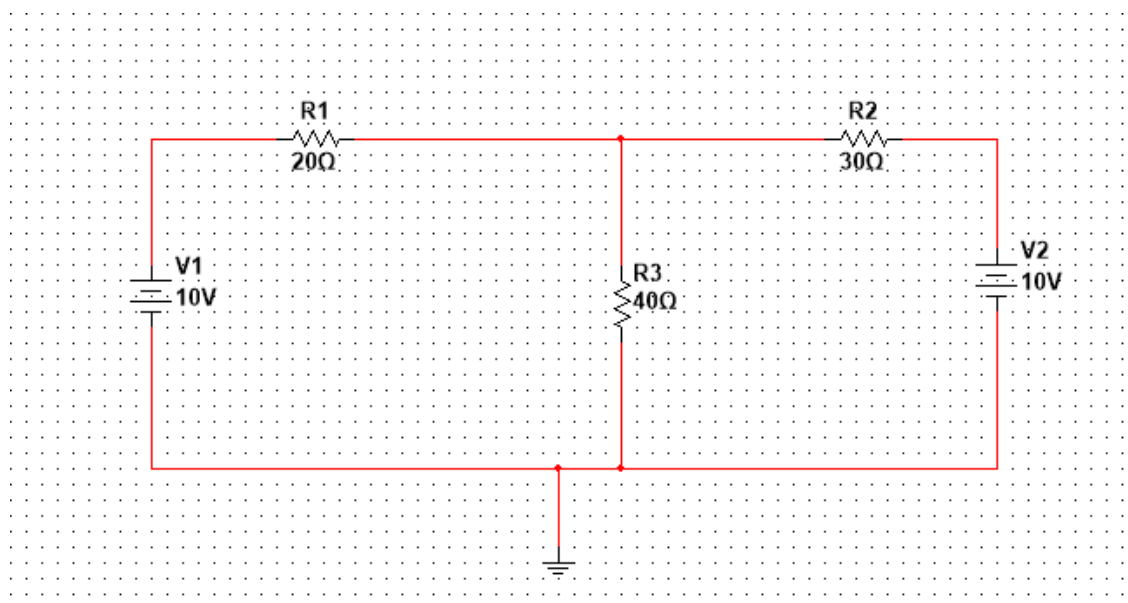**Circuit Diagram :**

**Result & Observations :**

<b>Parameter</b>	<b>Calculated Value</b>	<b>Average value</b>
Z <sub>11</sub>	60	59.998
Z <sub>21</sub>	40	40.001
Z <sub>12</sub>	40	39.998
Z <sub>22</sub>	70	70
Y <sub>11</sub>	0.0269	0.0269
Y <sub>21</sub>	0.0153	0.01538
Y <sub>12</sub>	0.0153	0.01538
Y <sub>22</sub>	0.023	0.023
h <sub>11</sub>	37.142	37.14
h <sub>21</sub>	0.571	0.57
h <sub>12</sub>	0.571	0.571
h <sub>22</sub>	0.0142	0.0142
A	1.5	1.499
B	-65	-65
C	0.025	0.0249
D	-1.75	-1.75

Hence we can see that the calculated and experimental values match.  
Therefore all parameters of two port networks have been verified.

## EXPERIMENT-7


**Objective:** studying input and output characteristics of semiconductor diodes

**Software used:** NI Multisim 14.0


**Theory:** A semiconductor diode is a combination of p and n type semiconductors which in forward bias conducts current only above a certain voltage known as cutting voltage. After achieving cutting voltage, the increase in current is almost exponential. A diode in reverse bias conducts negligible amount of current in the order of micro amperes.

**Circuit diagrams:**


➤ **Forward bias diode**

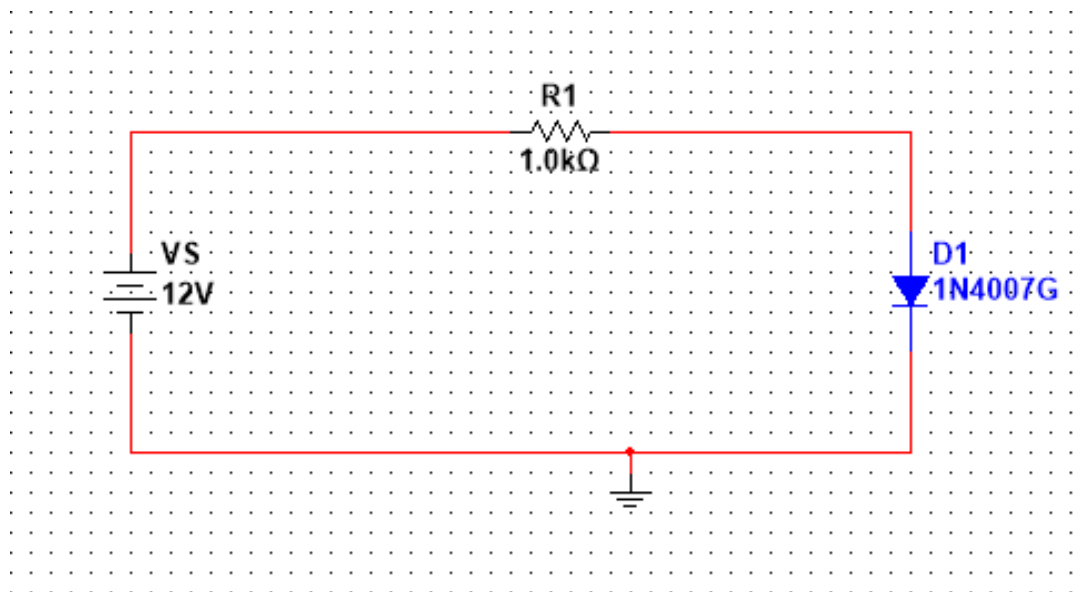

➤ Reverse bias diode

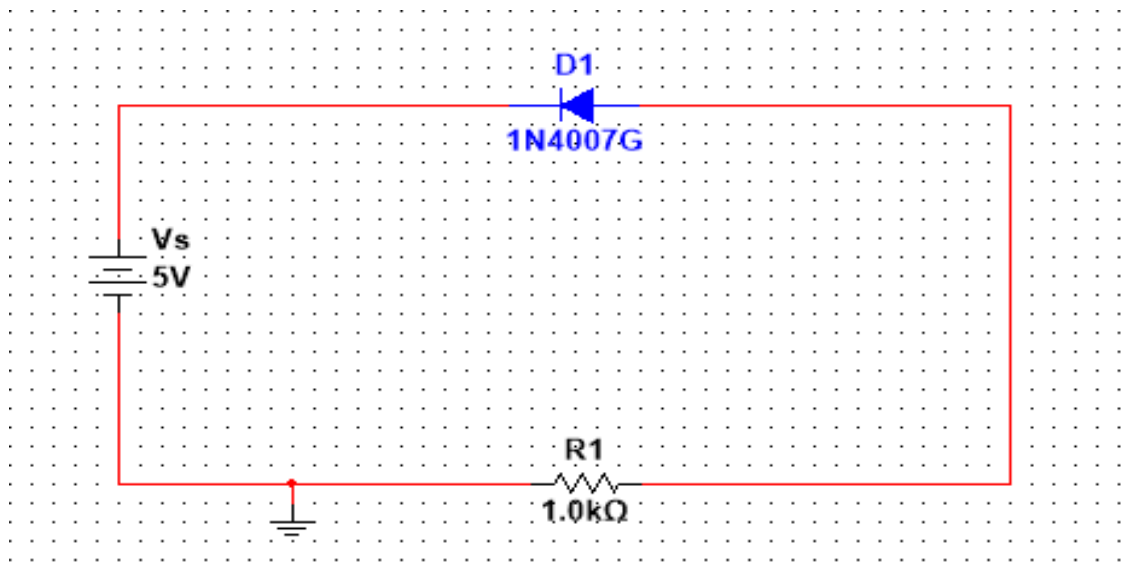


➤ Common emitter configuration

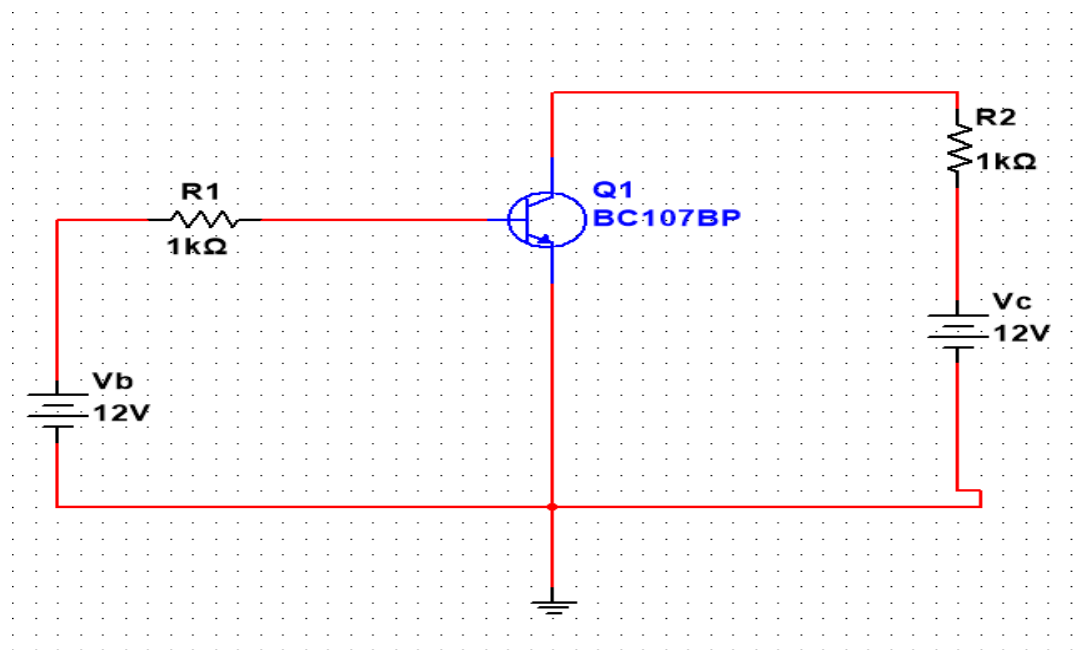


Result and observation:

➤ Forward bias graph

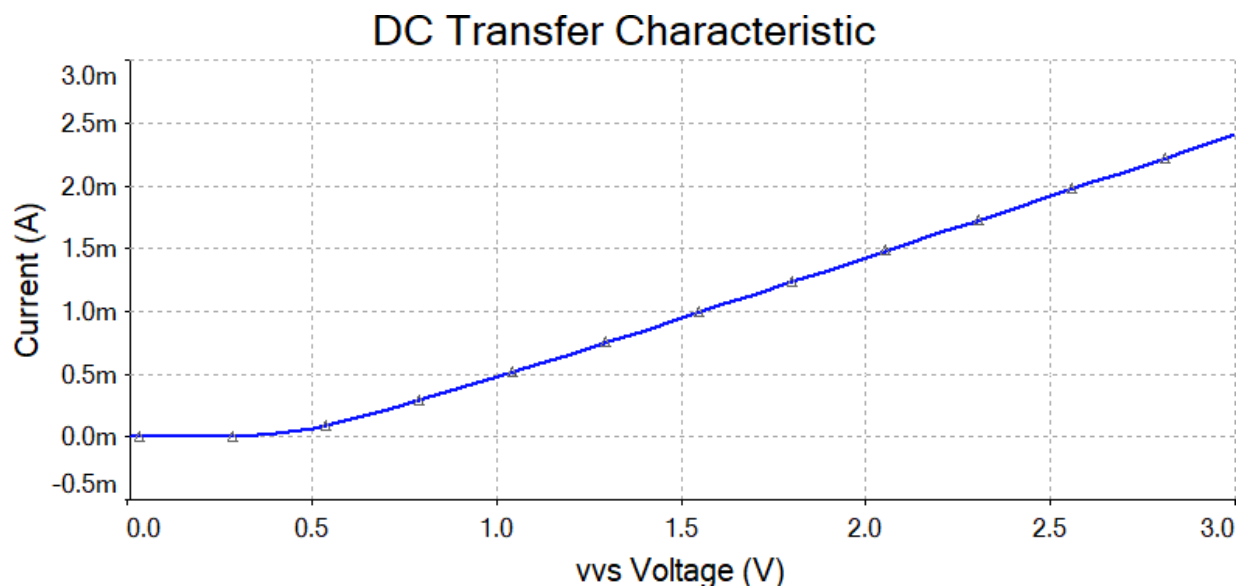

Cutting voltage for forward bias graph is 0.3V. Hence it is germanium diode

➤ Reverse bias graph

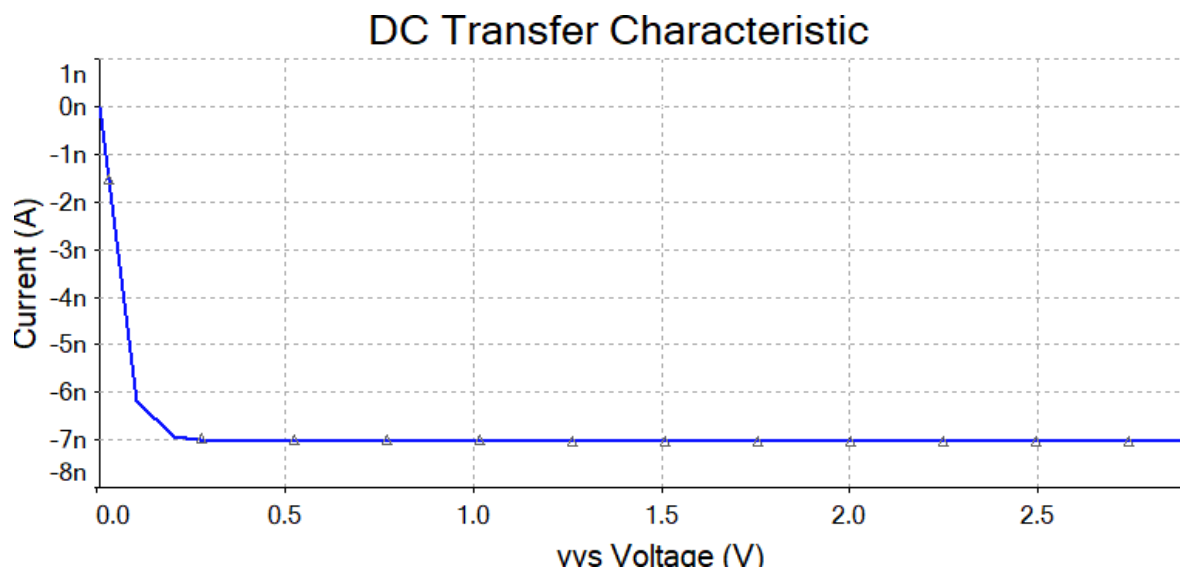


The leakage current is zero or negligible




➤ Common emitter input characteristics

DC Transfer Characteristic

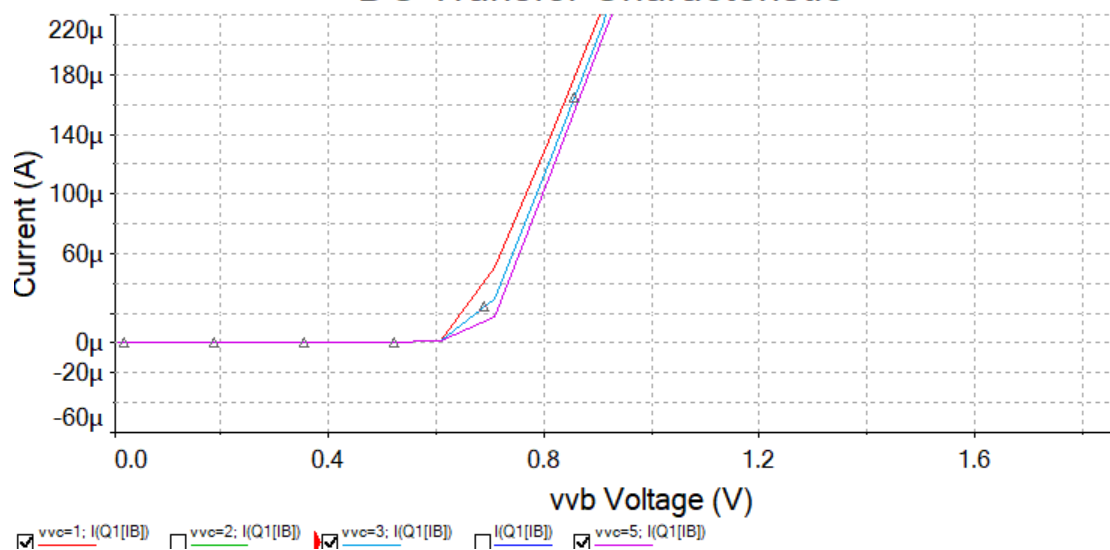

	Voltage(vc)		
	1V	3V	5V
<b>Cutting voltage (V<sub>y</sub>)</b>	<b>0.500V</b>	<b>0.506V</b>	<b>0.510V</b>

➤ Common emitter output characteristics

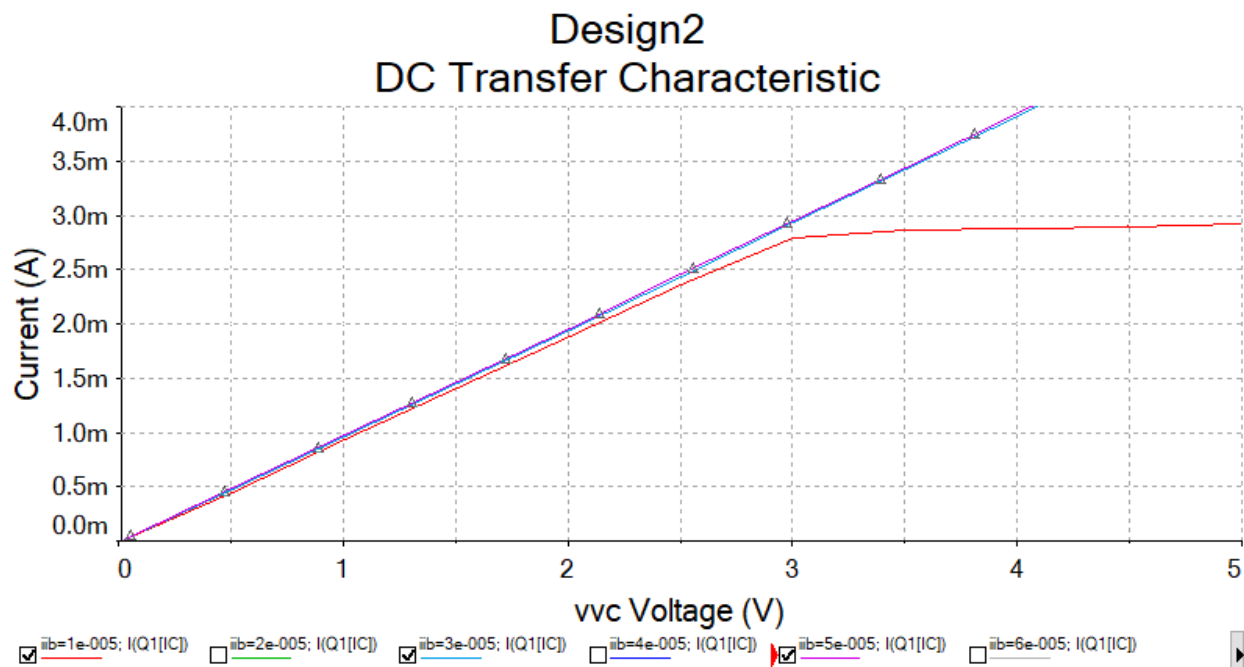

	Base current( $I_b$ )		
	10 $\mu$ A	30 $\mu$ A	50 $\mu$ A
<b>Collector voltage (<math>I_c</math>)</b>	<b>2.77mA</b>	<b>8.74mA</b>	<b>14.46mA</b>

## **Experiment 8**

**Objective:** To design and simulate various rectifier circuits.

**Software used:** Ni Multisim 14.0

**Theory:** A rectifier is a device that converts an oscillating two-directional alternating current (AC) into a single-directional direct current (DC). Rectifiers can take a wide variety of physical forms, from vacuum tube diodes and crystal radio receivers to modern silicon-based designs

There are two types of rectifier


- Half wave rectifier
- Full wave rectifier

**Half wave rectifier:** For most power applications, half-wave rectification is insufficient for the task. The harmonic content of the rectifier's output waveform is very large and consequently difficult to filter. Furthermore, the AC power source only supplies power to the load one half every full cycle, meaning that half of its capacity is unused. Half-wave rectification is, however, a very simple way to reduce power to a resistive load. Some two-position lamp dimmer switches apply full AC power to the lamp filament for "full" brightness and then half-wave rectify it for a lesser light output.


**Full wave rectifier:** if we need to rectify AC power to obtain the full use of both half cycles of the sine wave, a different rectifiers circuit configuration must be used. Such a circuit is called a full-wave rectifier. One kind of full-wave rectifier, called the center-tap design, uses a transformer with a center-tapped secondary winding and two diodes

## Circuit diagram

- Half wave rectifier:

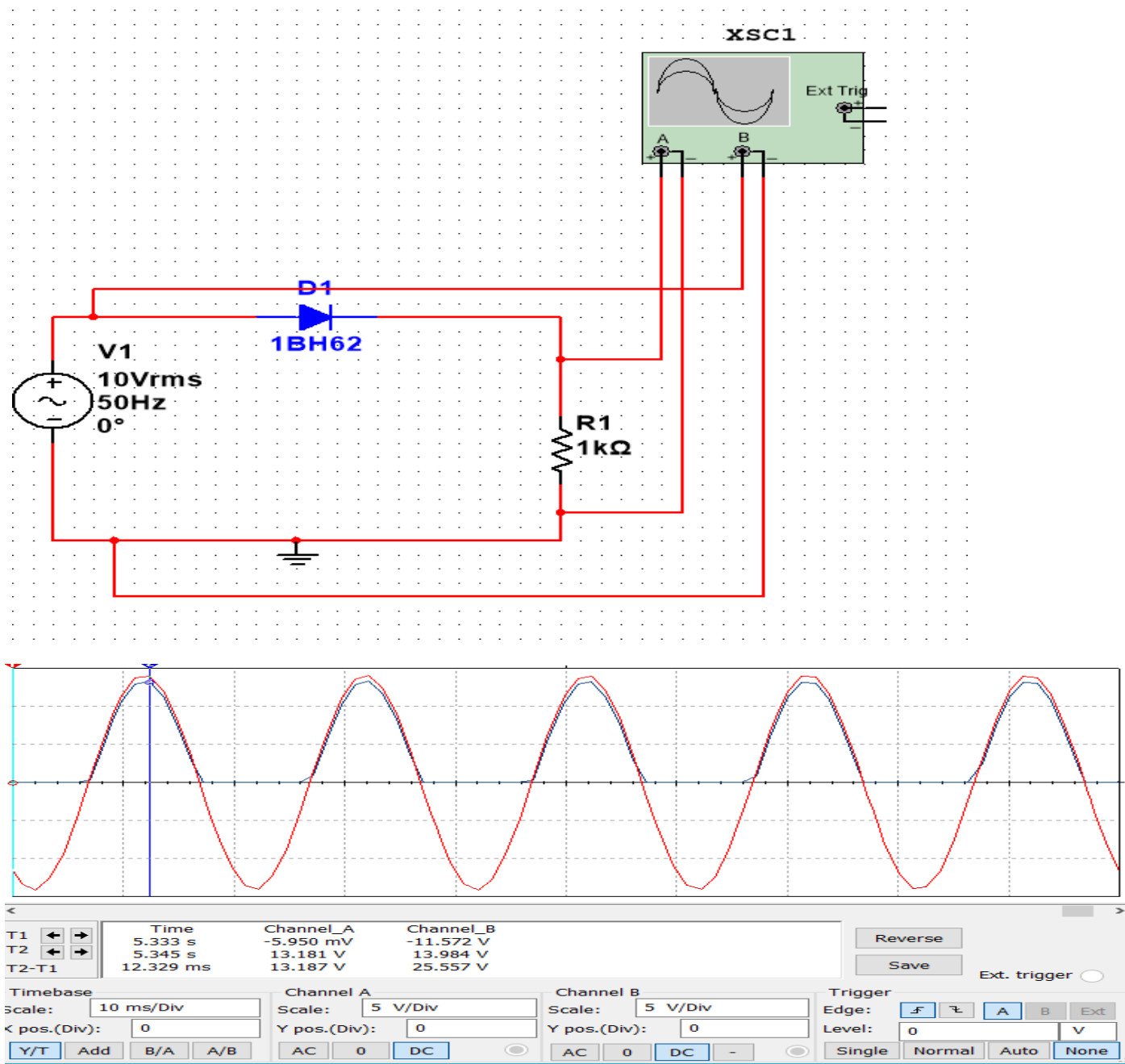

- Full wave rectifier:

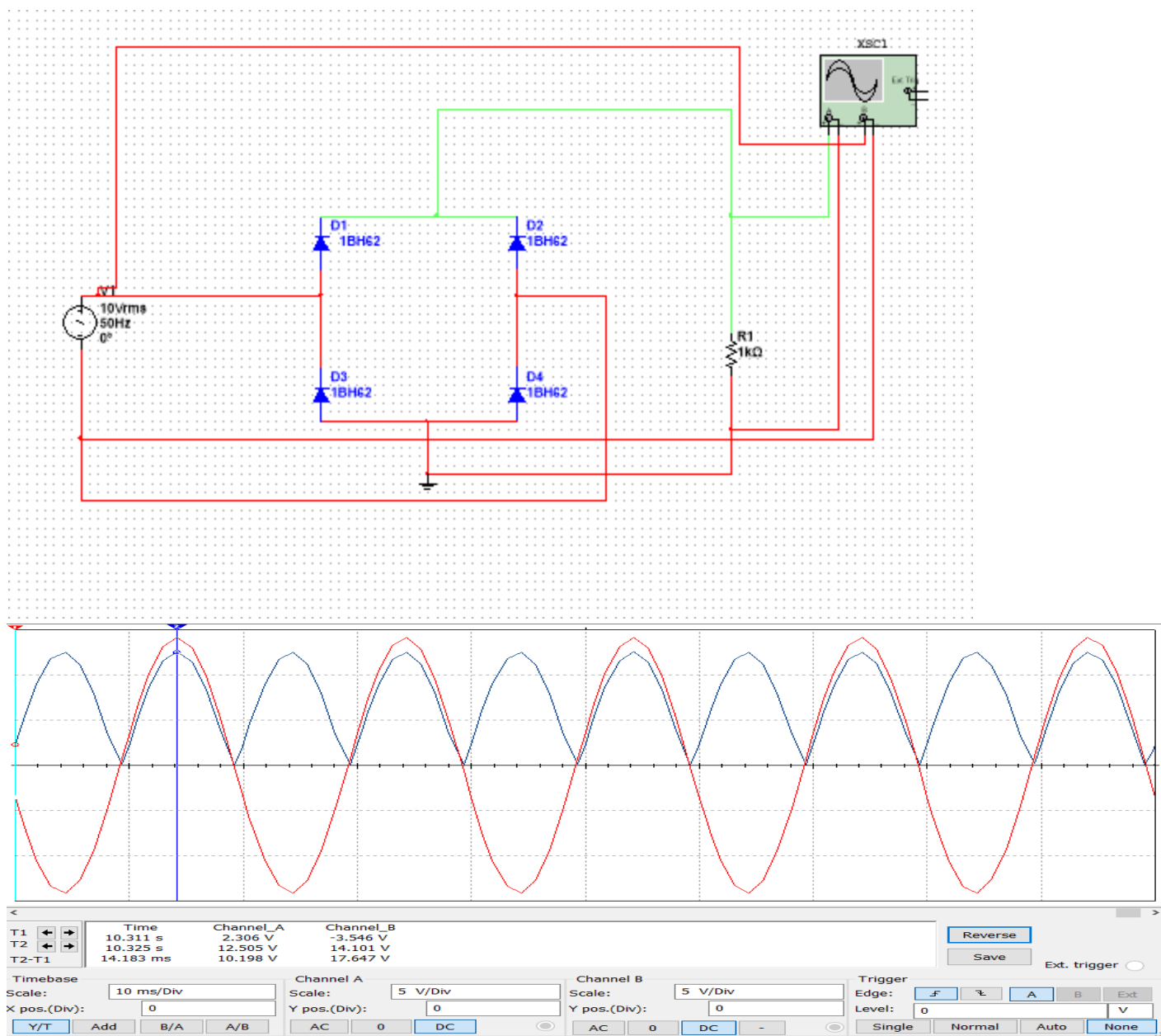

### Result and observation:

#### half wave rectifier:

VM		VRMS		VDC		Ripple factor ( $\gamma$ )	
Theory	Multisim	Theory	Multisim	Theory	Multisim	Theory	Multisim
20	13.181	10	6.590	6.636	4.195	1.2114	1.2115

#### Full wave rectifier:

VM		VRMS		VDC		Ripple factor ( $\gamma$ )	
Theory	Multisim	Theory	Multisim	Theory	Multisim	Theory	Multisim
14.14	12.505	10	8.843	9.001	7.960	0.484	0.483

Hence we saw that theoretical and multisim values are same the experiment has proved

## EXPERIMENT -9

### MOSFET AMPLIFIER

**AIM:**


To study the MOSFET amplifier working in common source configuration with given specifications.

**THEORY:**


The MOSFET structure has become the most important device structure in the electronics industry. It dominates the integrated circuit technology in Very Large Scale Integrated (VLSI) digital circuits based on n-channel MOSFETs and Complementary n- channel and p-channel MOSFETs (CMOS). The technical importance of the MOSFET results from its low power consumption, simple geometry, and small size, resulting in very high packing densities and compatibility with VLSI manufacturing technology. Two of the most popular configurations of small-signal MOSFET amplifiers are the common source and common drain configurations. The common source circuit is shown below. The common sources, like all MOSFET amplifiers, have the characteristic of high input impedance. High input impedance is desirable to keep the amplifier from loading the signal source. This high input impedance is controlled by the bias resistors  $R_1$  and  $R_2$ ). Normally the value of the bias resistors is chosen as high as possible. However, too big a value can cause a significant voltage drop due to the gate leakage current. A large voltage drop is undesirable because it can disturb the bias point. For

amplifier operation the MOSFET should be biased in the active region of the characteristics.

### CIRCUIT DIAGRAM:

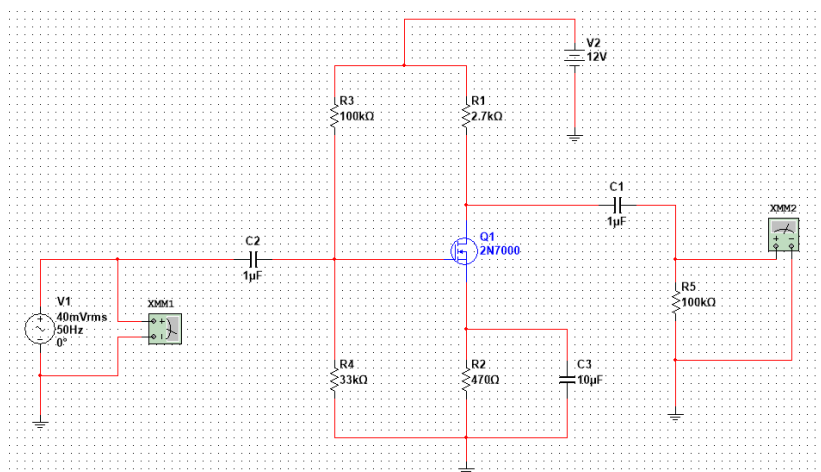

### RESULT & OBSERVATION:

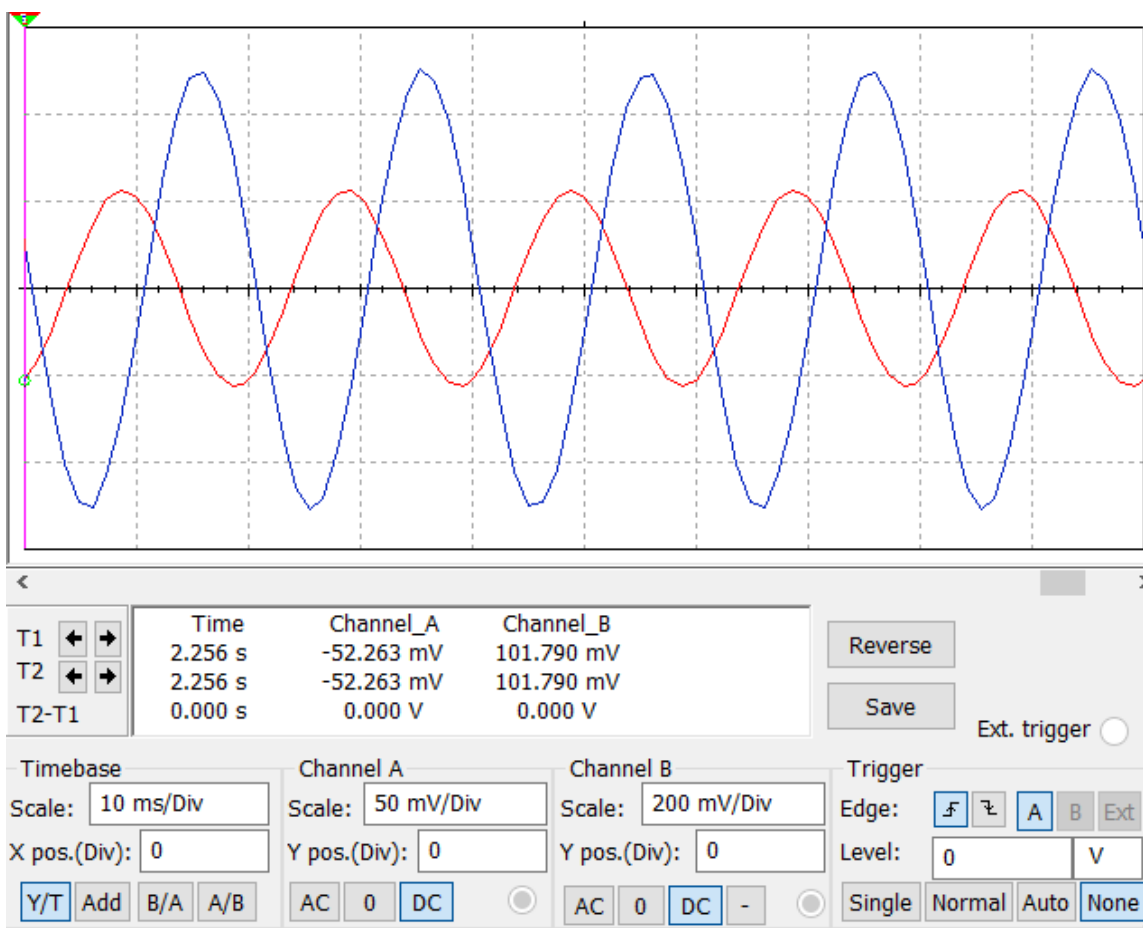



INPUT VOLTAGE $V_i$ (mV)	OUTPUT VOLTAGE $V_o$ (mV)	VOLTAGE GAIN $V_o/V_i$ (mV)
40.021	355.734	8.888
50.016	442.937	8.856

Therefore we can see the MOSFET given an voltage gain of 8.8  
Such that MOSFET works as an voltage amplifier

## Experiment – 10


### APPLICATION OF THEVENIN'S THEOREM

**Objective:** To Verify Thevenin's theorem.


**Software Used:** NI Multisim 14.0

**Circuit diagrams:**


Overall circuit

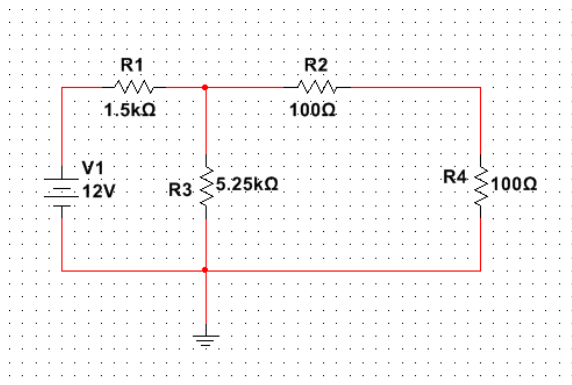

Circuit for  $V_{th}$

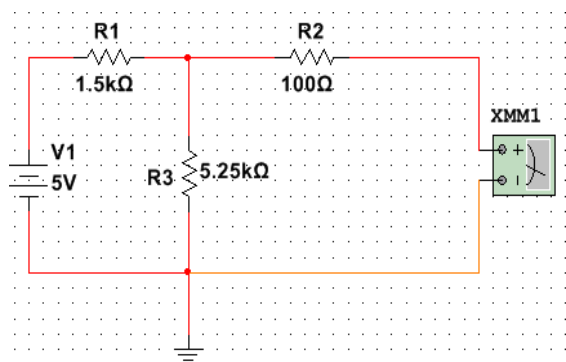

### Circuit for R<sub>th</sub>

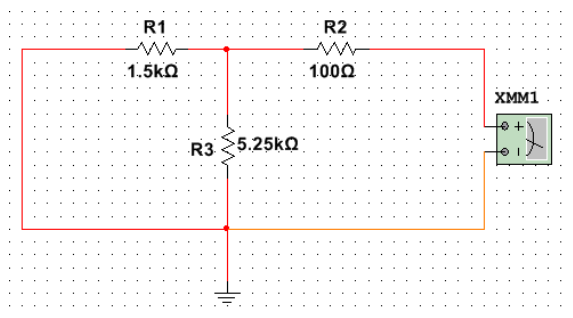

### Theory:

Any linear, bilateral network having a number of voltage, current sources and resistances can be replaced by a simple equivalent circuit consisting of a single voltage source in series with a resistance, where the value of the voltage source is equal to the open circuit voltage and the resistance is the equivalent resistance measured between the open circuit terminals with all energy sources replaced by their ideal internal resistances.

### Result & Observations :

				$V_{Th}$		$R_{Th}$	
$V_s$	$R_1$	$R_2$	$R_3$	Theoretical	Multisim	Theoretical	Multisim
5V	1.2kΩ	1 kΩ	1.3k Ω	2.6V	2.6V	1.624k Ω	1.624k Ω
5.2V	3k Ω	1 kΩ	4k Ω	4.571V	4.571V	2.7142k Ω	2.714k Ω
7.6V	7k Ω	5kΩ	4kΩ	2.764V	2.764V	7.5454k Ω	7.545k Ω
10V	9.5k Ω	6.2kΩ	2.4kΩ	2.017V	2.017V	8.116k Ω	8.116k Ω

Hence we can see the match of multisim and theoretical values we can say this experiment is proved

# **END OF LAB REPORT**

# **THANK YOU**

**DONE BY**

**MAJJIGA JASWANTH**

**20BCD7171**